

AM Receivers

Superheterodyne Receivers

Typical receiver circuits include:


- RF amplifiers
- IF amplifiers
- Mixer

RF Amplifier

RF Input Amplifier

- The RF amplifier, also called a low-noise amplifier (LNA), processes the very weak input signals, increasing their amplitude prior to mixing.
- Low-noise components are used to ensure a sufficiently high S/N ratio.
- Selectivity should be such that it effectively eliminates images.
- The RF amplifier is typically a class A circuit that can be configured with bipolar or field-effect transistors.

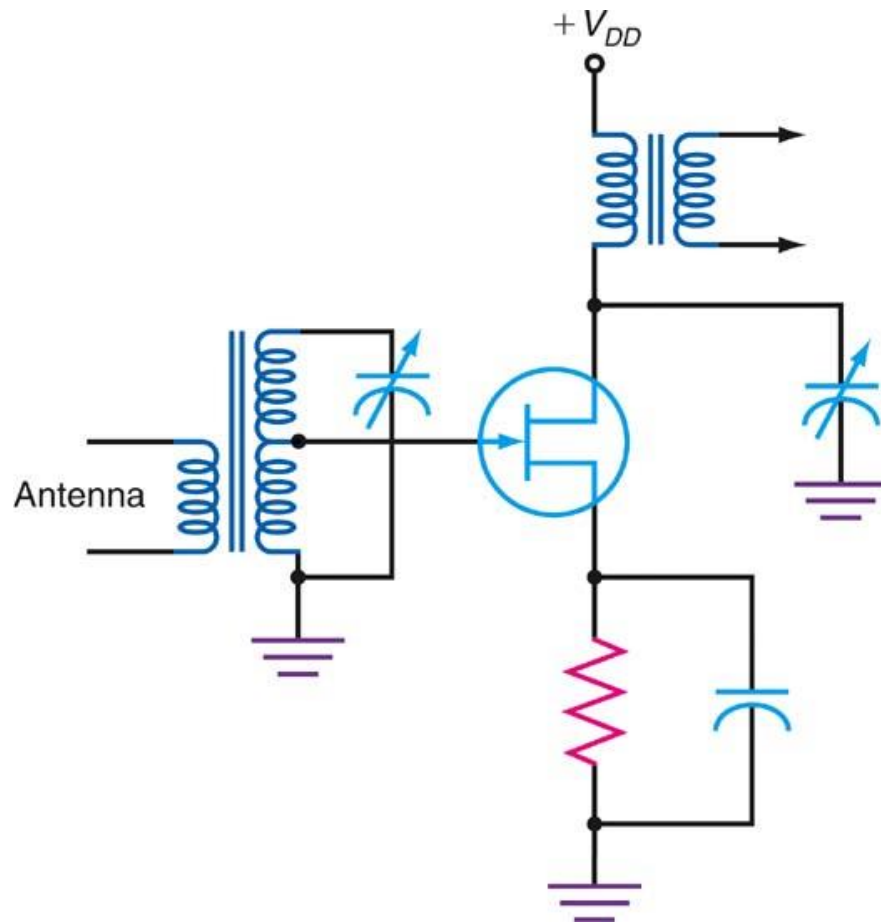
- ❑ Class A amplifier capable of providing gain in the 10- to 30-dB range.




Class A RF amplifier

IF Amplifier

- The detailed circuitry of the IF amplifier may differ from one system to another, it always has a tuned (resonant) circuit on the input or on the output or on both.
- The **IF** amplifier is a frequency-selective circuit, it responds only to **455 kHz** and any side frequencies lying in the **10 kHz** band centered at 455 kHz. All of the frequencies out of the mixer are rejected **except** the 455 kHz IF, all lower-side frequencies down to 450 kHz, and all upper-side frequencies up to 460 kHz. This frequency spectrum is the audio modulated intermediate frequency

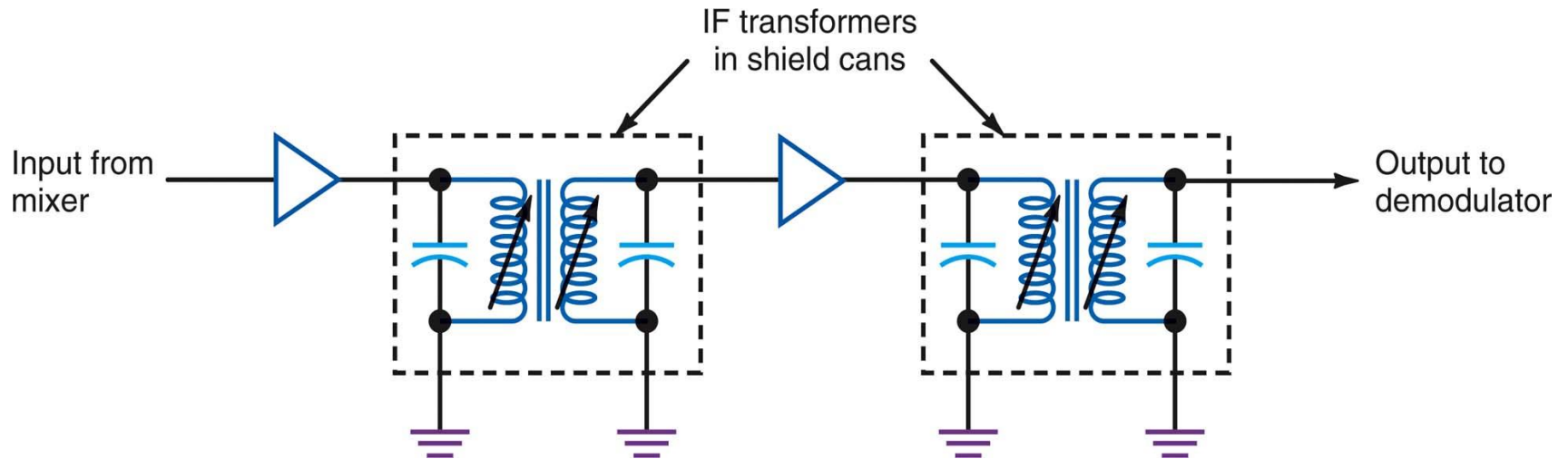


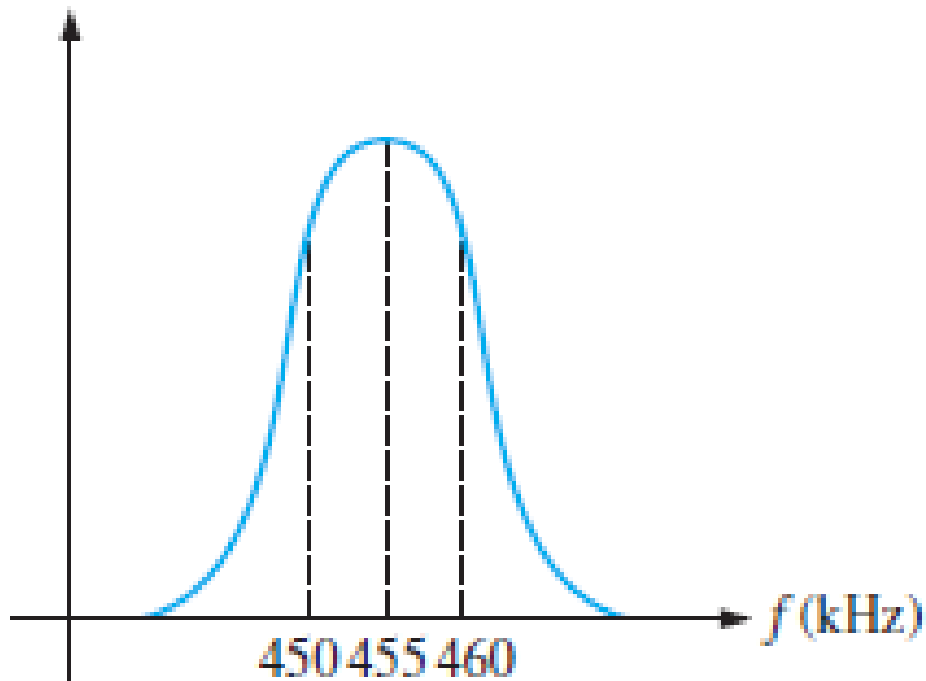A two-stage IF amplifier using double-tuned transformer coupling for selectivity.



IF Frequency response curve

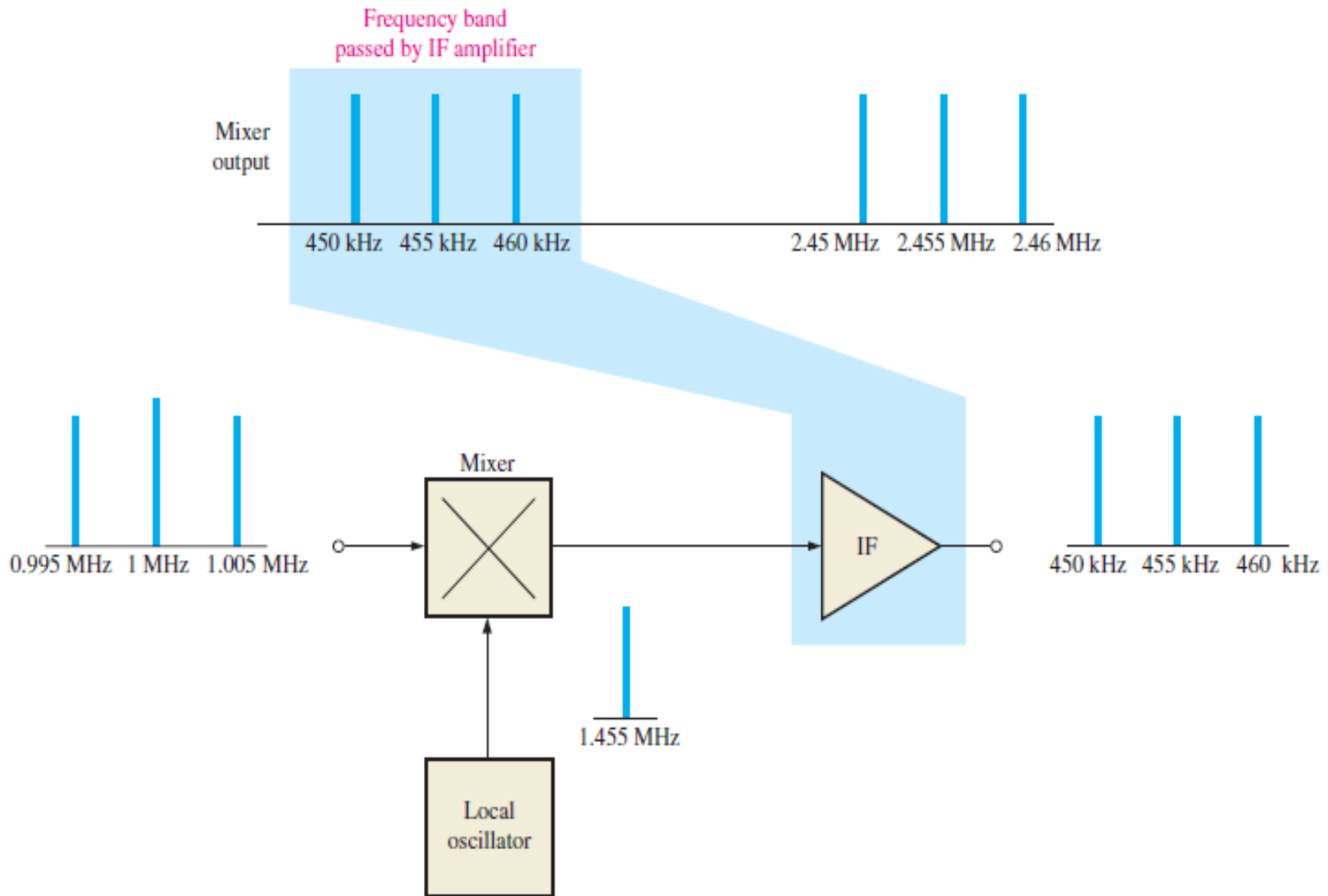- Most of the gain and selectivity in a superheterodyne receiver are obtained in the IF amplifier.
- Usually two or more IF amplifiers are used to provide adequate receiver gain.




An illustration of the basic function of the IF amplifier in an AM receiver.

MIXER

- The primary characteristic of mixer circuits is nonlinearity.
- Any device or circuit whose output does not vary linearly with the input can be used as a mixer.
- One of the most widely used types of mixer is the simple diode modulator.

Diode Mixer

- The input signal is applied to the primary winding of the transformer.
- The signal is coupled to the secondary winding and applied to the diode mixer, and the local oscillator signal is coupled to the diode by way of a capacitor.
- The input and local oscillator signals are linearly added and applied to the diode, which produces the sum and difference frequencies.
- The output signals are developed across the tuned circuit which selects the difference frequency.

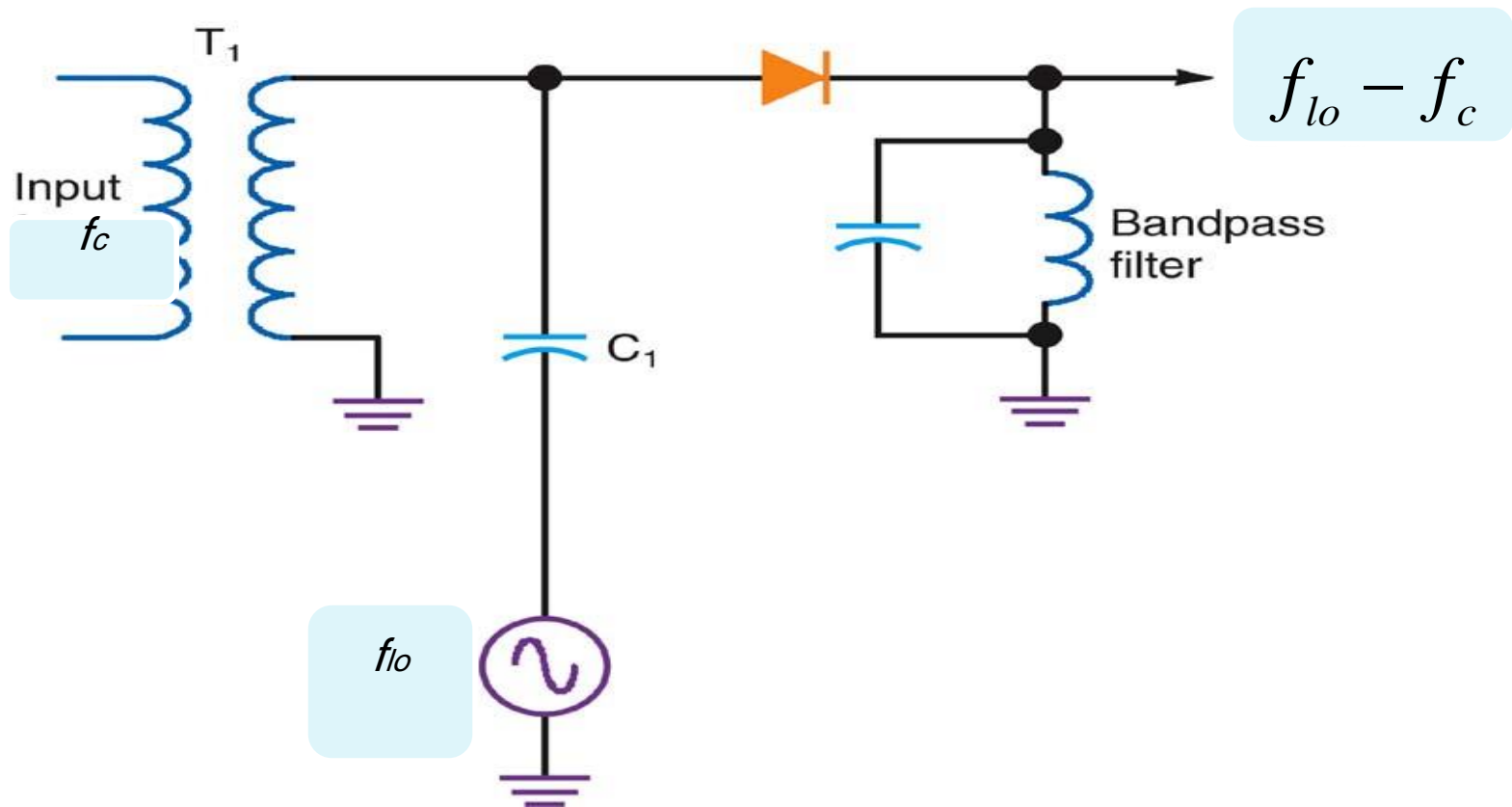

Circuit of diode mixer.


Image Problem

Solving the Image Problem

- To reduce image interference, high- Q tuned circuits should be used ahead of the mixer or RF amplifier.
- The **IF** is made as high as possible for effective elimination of the image problem, yet low enough to prevent design problems.
- In most receivers the IF varies in proportion to the frequencies that must be covered.

Dual-Conversion Receivers

- ❖ Another way to obtain selectivity while eliminating the image problem is to use a **dual-conversion superheterodyne receiver**.
- ❖ A typical receiver uses two mixers and local oscillators, so it has two IFs.
- ❖ The first mixer converts the incoming signal to a high intermediate frequency to eliminate the images.
- ❖ The second mixer converts that IF down to a much lower frequency, where good selectivity is easier to obtain.

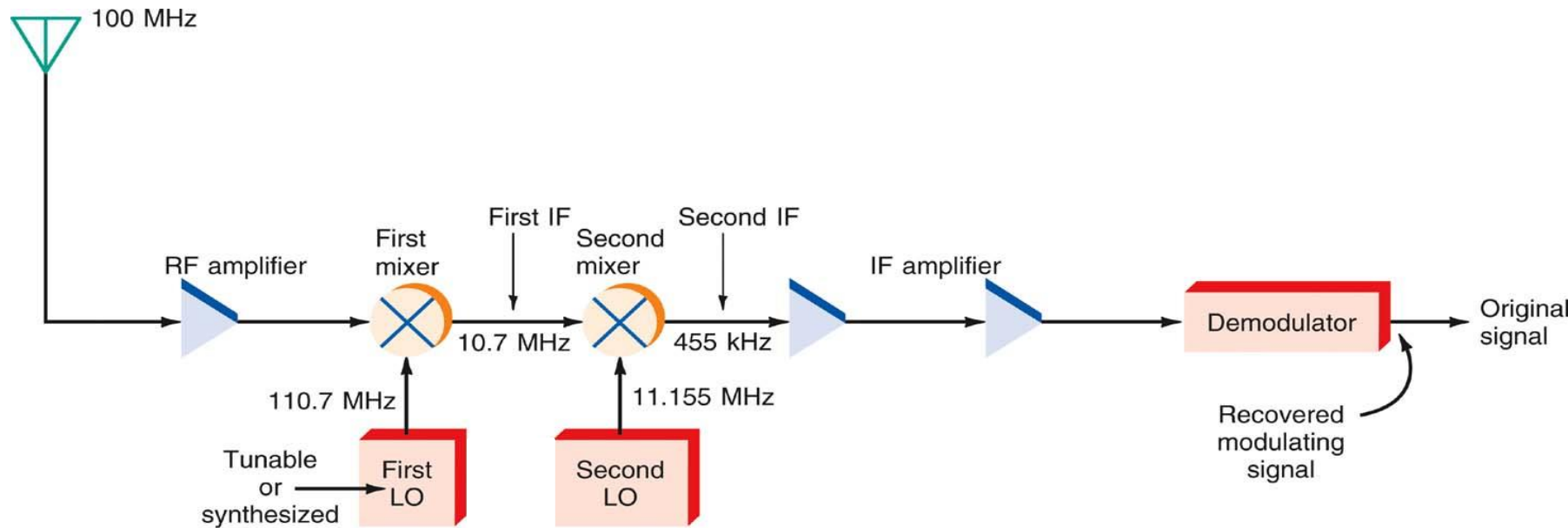

A dual-conversion superheterodyne